















Name	Value
 a	0
 b	1
 cin	1
▼  o[7:0]	40
 [7]	0
 [6]	1
 [5]	0
 [4]	0
 [3]	0
 [2]	0
 [1]	0
 [0]	0
 s	0
 ca	1



fa_2to4decoder - [C:/Users/raghava guptha/fa_2to4decoder/fa_2to4decoder.xpr] - Vivado 2023.2

File Edit Flow Tools Reports Window Layout View Help Q- Quick Access

 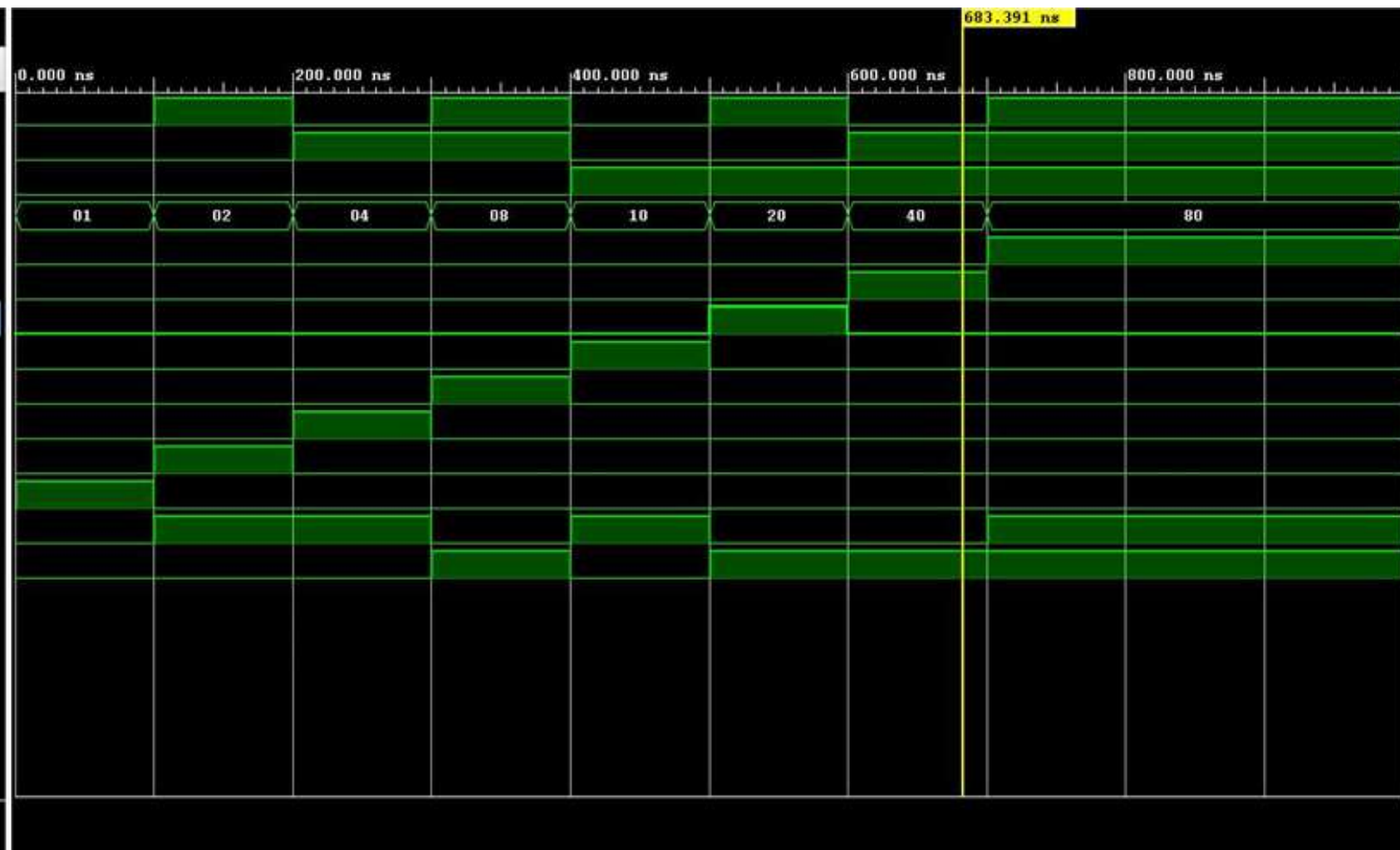Ready

Default Layout

Flow Navigator

- PROJECT MANAGER
 - Settings
 - Add Sources
 - Language Templates
 - IP Catalog
- IP INTEGRATOR
 - Create Block Design
 - Open Block Design
 - Generate Block Design
- SIMULATION
 - Run Simulation
- RTL ANALYSIS
 - Run Linter
 - Open Elaborated Design
 - Report Methodology
 - Report DRC
 - Report Noise
 - Schematic

ELABORATED DESIGN - xc7a35tcpg236-1

Project Summary x Schematic x fa_2to4decoder.v* x

9 Cells 13 I/O Ports 18 Nets

The schematic diagram illustrates a 2-to-4 decoder circuit. It features two 2-to-4 decoders, d1 and d2, and three RTL_OR blocks. The inputs are b, a, and cin. b and a are connected to the 'a' and 'b' inputs of d1 and d2. cin is connected to the 'en' input of d1 and the 'en0_i' input of an RTL_INV block. The output of RTL_INV is connected to the 'en' input of d2. The outputs of d1 and d2 are connected to the inputs of three RTL_OR blocks. The outputs of these RTL_OR blocks are connected to the inputs of three more RTL_OR blocks, which produce the final outputs: ca, o[7:0], and s.

Tcl Console Messages Log Reports Design Runs

fa_2to4decoder - [C:/Users/raghava guptha/fa_2to4decoder/fa_2to4decoder.xpr] - Vivado 2023.2

FileEditFlowToolsReportsWindowLayoutViewHelpQ- Quick Access

Ready

Default Layout

Flow Navigator

PROJECT MANAGER

Settings

Add Sources

Language Templates

IP Catalog

IP INTEGRATOR

Create Block Design

Open Block Design

Generate Block Design

SIMULATION

Run Simulation

RTL ANALYSIS

Run Linter

Open Elaborated Design

Report Methodology

Report DRC

Report Noise

Schematic

ELABORATED DESIGN - xc7a35tcbg236-1

Sources

Netlist

Source File Properties

Project Summary

Schematic

fa_2to4decoder.v *

C:/Users/raghava guptha/fa_2to4decoder/fa_2to4decoder.srscs/sources_1/new/fa_2to4decoder.v

7

begin

8

case({a, b})

9

2'b00: o = 4'b0001;

10

2'b01: o = 4'b0010;

11

2'b10: o = 4'b0100;

12

2'b11: o = 4'b1000;

13

endcase

14

end

15

else

16

o = 4'b0000;

17

end

18

endmodule

19

module fa_dec2to4(a, b, cin, o, s, ca);

20

input a, b, cin;

21

output [7:0] o;

22

output reg s, ca;

23

24

dec_2to4 d1(b, a, ~cin, o[3:0]);

25

dec_2to4 d2(b, a, cin, o[7:4]);

26

always @(*)

27

begin

28

s = o[1] | o[2] | o[4] | o[7];

29

ca = o[3] | o[5] | o[6] | o[7];

30

end

31

endmodule

Tcl Console

Messages

Log

Reports

Design Runs

83°F

Partly cloudy

Search

ENG IN

1:5

Insert

Verilog

7:40 PM

6/15/2025

fa_2to4decoder - [C:/Users/raghava guptha/fa_2to4decoder/fa_2to4decoder.xpr] - Vivado 2023.2

FileEditFlowToolsReportsWindowLayoutViewHelpQ- Quick Access

Ready

Default Layout

Flow Navigator

PROJECT MANAGER

Settings

Add Sources

Language Templates

IP Catalog

IP INTEGRATOR

Create Block Design

Open Block Design

Generate Block Design

SIMULATION

Run Simulation

RTL ANALYSIS

Run Linter

Open Elaborated Design

Report Methodology

Report DRC

Report Noise

Schematic

ELABORATED DESIGN - xc7a35tcbg236-1

Sources

Netlist

Source File Properties

Project Summary x

Schematic x

fa_2to4decoder.v * x

C:/Users/raghava guptha/fa_2to4decoder/fa_2to4decoder.srcs/sources_1/new/fa_2to4decoder.v

1 module dec_2to4(a, b, en, o);

2 input a, b, en;

3 output reg [3:0] o;

4 always @(*)

5 begin

6 if (en == 1'b1)

7 begin

8 case({a, b})

9 2'b00: o = 4'b0001;

10 2'b01: o = 4'b0010;

11 2'b10: o = 4'b0100;

12 2'b11: o = 4'b1000;

13 endcase

14 end

15 else

16 o = 4'b0000;

17 end

18 endmodule

19 module fa_dec2to4(a, b, cin, o, s, ca);

20 input a, b, cin;

21 output [7:0] o;

22 output reg s, ca;

23

24 dec_2to4 d1(b, a, ~cin, o[3:0]);

25 dec_2to4 d2(b, a, cin, o[7:4]);

Tcl Console

Messages

Log

Reports

Design Runs

83°F

Partly cloudy

Search

ENG IN

1:5

Insert

Verilog

7:40 PM

6/15/2025



ha_2to4decoder - [C:/Users/raghava guptha/ha_2to4decoder/ha_2to4decoder.xpr] - Vivado 2023.2

File Edit Flow Tools Reports Window Layout View Help Q- Quick Access

Ready

Default Layout

Flow Navigator

ELABORATED DESIGN - xc7a35tcpg236-1

Project Summary x Schematic x ha_2to4decoder.v * x

2 Cells 9 I/O Ports 8 Nets

Source File Properties

RTL ANALYSIS

Run Linter

Open Elaborated Design

Report Methodology

Report DRC

Report Noise

Schematic

Tcl Console Messages Log Reports Design Runs

ha_2to4decoder - [C:/Users/raghava guptha/ha_2to4decoder/ha_2to4decoder.xpr] - Vivado 2023.2

FileEditFlowToolsReportsWindowLayoutViewHelpQ- Quick Access

Ready

Default Layout

Flow Navigator

PROJECT MANAGER

Settings

Add Sources

Language Templates

IP Catalog

IP INTEGRATOR

Create Block Design

Open Block Design

Generate Block Design

SIMULATION

Run Simulation

RTL ANALYSIS

Run Linter

Open Elaborated Design

Report Methodology

Report DRC

Report Noise

Schematic

ELABORATED DESIGN - xc7a35tcbg236-1

Project SummarySchematicha_2to4decoder.v*

C:/Users/raghava guptha/ha_2to4decoder/ha_2to4decoder.srsrcs/sources_1/new/ha_2to4decoder.v

1module dec_2to4(a, b, en, c);
2input a, b, en;
3output reg [3:0] c;
4always @(*)
5begin
6if (en == 1'b1)
7begin
8case({a, b})
92'b00: c = 4'b0001;
102'b01: c = 4'b0010;
112'b10: c = 4'b0100;
122'b11: c = 4'b1000;
13default: c = 4'b0000;
14endcase
15end
16else
17c = 4'b0000;
18end
19endmodule
20
21module ha_dec2to4(a, b, en, c, s, ca);
22input a, b, en;
23output [3:0] c;
24output s, ca;
25dec_2to4 d(a, b, en, c);
26

Tcl ConsoleMessagesLogReportsDesign Runs

83°F
Partly cloudy

Search

24:5
Insert
Verilog

7:37 PM
6/15/2025