



half\_sub - [C:/Users/raghava guptha/half\_sub/half\_sub.xpr] - Vivado 2023.2

File Edit Flow Tools Reports Window Layout View Help Q- Quick Access

Ready

Default Layout

Flow Navigator

- PROJECT MANAGER
  - Settings
  - Add Sources
  - Language Templates
  - IP Catalog
- IP INTEGRATOR
  - Create Block Design
  - Open Block Design
  - Generate Block Design
- SIMULATION
  - Run Simulation
- RTL ANALYSIS
  - Run Linter
  - Open Elaborated Design
    - Report Methodology
    - Report DRC
    - Report Noise
    - Schematic

ELABORATED DESIGN - xc7a35tcbg236-1

Project Summary x Schematic x half\_sub.v x

3 Cells 4 I/O Ports 6 Nets

The schematic diagram shows a half-subtractor circuit. It consists of two 2-to-1 multiplexers, m1 and m2, and an RTL\_INV block. Input 'b' is connected to a multiplexer (black diamond) and the 'i0' input of the RTL\_INV block. The output of the multiplexer is connected to the 'i0' input of the RTL\_INV block. The output of the RTL\_INV block is connected to the 'i[1:0]' input of both m1 and m2. The 's' input of both m1 and m2 is connected to the output of the RTL\_INV block. The 'y' output of m1 is connected to the 'diff' output, and the 'y' output of m2 is connected to the 'bo' output. A ground symbol is connected to the 's' input of m2.

half\_sub - [C:/Users/raghava guptha/half\_sub/half\_sub.xpr] - Vivado 2023.2

FileEditFlowToolsReportsWindowLayoutViewHelpQ- Quick Access

Ready

Default Layout

Flow Navigator

PROJECT MANAGER

Settings

Add Sources

Language Templates

IP Catalog

IP INTEGRATOR

Create Block Design

Open Block Design

Generate Block Design

SIMULATION

Run Simulation

RTL ANALYSIS

Run Linter

Open Elaborated Design

Report Methodology

Report DRC

Report Noise

Schematic

ELABORATED DESIGN - xc7a35tcpg236-1

Sources

Netlist

Source File Properties

Project Summary xSchematic xhalf\_sub.v x

C:/Users/raghava guptha/half\_sub/half\_sub.srsrcs/sources\_1/new/half\_sub.v

Q

1 module m\_2tol(i, s, y);

2 input [1:0] i;

3 input s;

4 output reg y;

5

6 always @(\*)

7 begin

8 case(s)

9 1'b0: y = i[0];

10 1'b1: y = i[1];

11 endcase

12 end

13 endmodule

14

15 module hs\_mux2tol(a, b, diff, bo);

16 input a, b;

17 output diff, bo;

18

19 m\_2tol m1({~b, b}, a, diff);

20 m\_2tol m2({1'b0, b}, a, bo);

21 endmodule

Tcl ConsoleMessagesLogReportsDesign Runs


85°F

Partly cloudy

Search

6:51 PM

6/15/2025

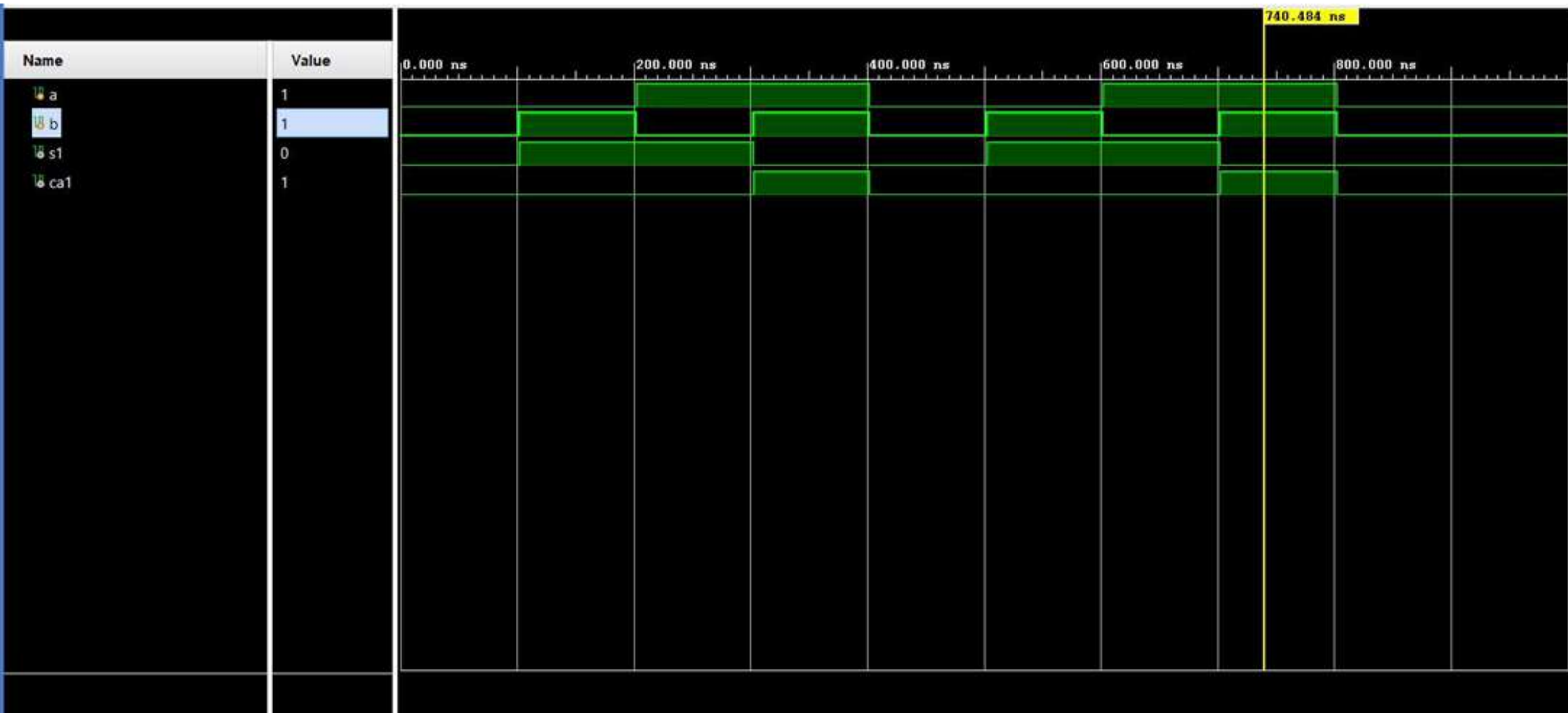

half\_adder - [C:/Users/raghava guptha/half\_adder/half\_adder.xpr] - Vivado 2023.2

File Edit Flow Tools Reports Window Layout View Help Q- Quick Access Ready

Flow Navigator

- PROJECT MANAGER
  - Settings
  - Add Sources
  - Language Templates
  - IP Catalog
- IP INTEGRATOR
  - Create Block Design
  - Open Block Design
  - Generate Block Design
- SIMULATION
  - Run Simulation
- RTL ANALYSIS
  - Run Linter
  - Open Elaborated Design
    - Report Methodology
    - Report DRC
    - Report Noise
    - Schematic

ELABORATED DESIGN - xc7a35tcbg236-1

Project Summary x Schematic x half\_adder.v x

3 Cells 4 I/O Ports 6 Nets

Tcl Console Messages Log Reports Design Runs

half\_adder - [C:/Users/raghava guptha/half\_adder/half\_adder.xpr] - Vivado 2023.2

File Edit Flow Tools Reports Window Layout View Help Q- Quick Access Ready

Flow Navigator

- PROJECT MANAGER
  - Settings
  - Add Sources
  - Language Templates
  - IP Catalog
- IP INTEGRATOR
  - Create Block Design
  - Open Block Design
  - Generate Block Design
- SIMULATION
  - Run Simulation
- RTL ANALYSIS
  - Run Linter
  - Open Elaborated Design
    - Report Methodology
    - Report DRC
    - Report Noise
    - Schematic

ELABORATED DESIGN - xc7a35tcbg236-1

Sources

Netlist


Source File Properties

Project Summary x Schematic x half\_adder.v x

C:/Users/raghava guptha/half\_adder/half\_adder.srscs/sources\_1/new/half\_adder.v

```
1 module mux_2to1(i, s, y);
2     input [1:0] i; // Fixed missing identifier
3     input s;
4     output reg y;
5
6     always @(*) begin // Fixed "always8" to "always @"
7         if (s == 0)
8             y = i[0]; // Fixed "[10]" to "i[0]"
9         else
10            y = i[1]; // Fixed "[1]" to "i[1]"
11        end
12    endmodule
13
14 module ha(a, b, s, ca);
15     input a, b;
16     output s, ca;
17
18     mux_2to1 m1({~b, b}, a, s); // Fixed "(-b,b)" to proper concatenation
19     mux_2to1 m2({b, 1'b0}, a, ca); // Fixed "1^b0" to "1'b0"
20 endmodule
```

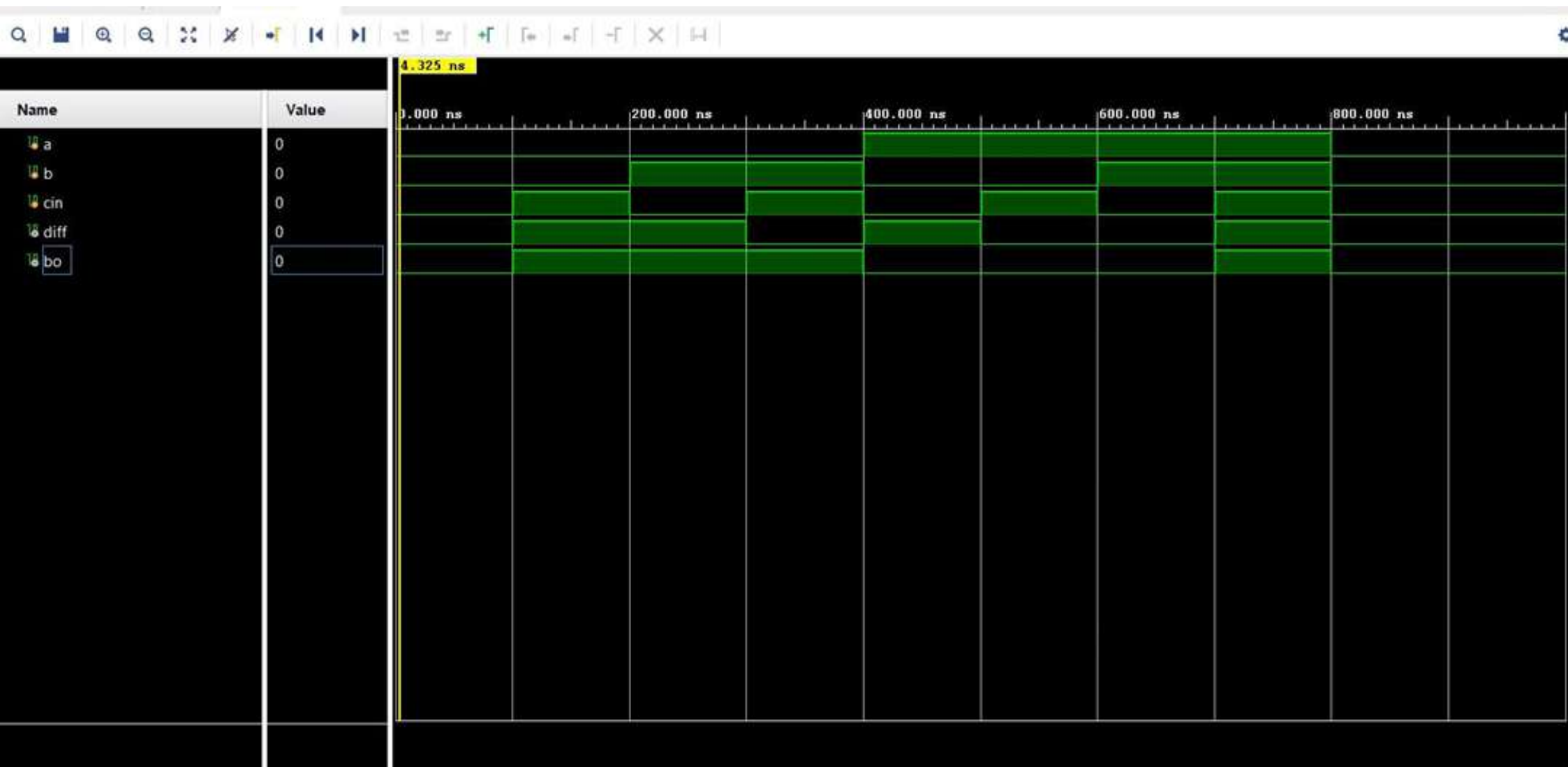Tcl Console Messages Log Reports Design Runs





fullsubtractor\_2to1 - [C:/Users/raghava guptha/fullsubtractor\_2to1/fullsubtractor\_2to1.xpr] - Vivado 2023.2

File Edit Flow Tools Reports Window Layout View Help Q- Quick Access

Ready

Default Layout

Flow Navigator

ELABORATED DESIGN - xc7a35tcbg236-1

Project Summary x Schematic x fullsub\_2to1.v x

7 Cells 5 I/O Ports 12 Nets

The schematic diagram illustrates a 2-bit full subtractor implemented using five 2-to-1 multiplexers (m1 to m5). The inputs are 'a' (2-bit), 'b' (2-bit), and 'cin' (1-bit). The circuit uses an RTL\_INV block to invert 'cin'. The outputs are 'diff' (2-bit) and 'bo' (1-bit). The multiplexers are configured as follows:

- m1: i[1:0] = b, s = cin, y = diff[1:0]
- m2: i[1:0] = b, s = cin, y = diff[1:0]
- m3: i[1:0] = b, s = cin, y = diff[1:0]
- m4: i[1:0] = b, s = cin, y = diff[1:0]
- m5: i[1:0] = b, s = cin, y = diff[1:0]

RTL\_ANALYSIS

- Run Linter
- Open Elaborated Design
- Report Methodology
- Report DRC
- Report Noise
- Schematic

Tcl Console Messages Log Reports Design Runs



fullsubtractor\_2to1 - [C:/Users/raghava guptha/fullsubtractor\_2to1/fullsubtractor\_2to1.xpr] - Vivado 2023.2

File Edit Flow Tools Reports Window Layout View Help Q Quick Access

Ready

Default Layout

Flow Navigator

PROJECT MANAGER

- Settings
- Add Sources
- Language Templates
- IP Catalog

IP INTEGRATOR

- Create Block Design
- Open Block Design
- Generate Block Design

SIMULATION

- Run Simulation

RTL ANALYSIS

- Run Linter
- Open Elaborated Design
  - Report Methodology
  - Report DRC
  - Report Noise
  - Schematic






ELABORATED DESIGN - xc7a35tcbg236-1


Project Summary x Schematic x fullsub\_2to1.v x

C:/Users/raghava guptha/fullsubtractor\_2to1/fullsubtractor\_2to1.srcs/sources\_1/new/fullsub\_2to1.v

```
1 module m2to1(i, s, y);
2     input [1:0] i;
3     input s;
4     output reg y;
5
6     always @(*)
7     begin
8         case(s)
9             1'b0: y = i[0];
10            1'b1: y = i[1];
11        endcase
12    end
13 endmodule
14
15 module fs_mux2to1(a, b, cin, diff, bo);
16     input a, b, cin;
17     output diff, bo;
18     wire [3:0] w;
19
20     m2to1 m1({~cin, cin}, b, w[0]);
21     m2to1 m2({cin, ~cin}, b, w[1]);
22     m2to1 m3({w[1], w[0]}, a, diff);
23     m2to1 m4({1'b1, cin}, b, w[2]);
24     m2to1 m5({cin, 1'b0}, b, w[3]);
25     m2to1 m6({w[3], w[2]}, a, bo);
26 endmodule
```

Tcl Console Messages Log Reports Design Runs

Name	Value
 a	0
 b	0
 cin	0
 s	0
 ca	0

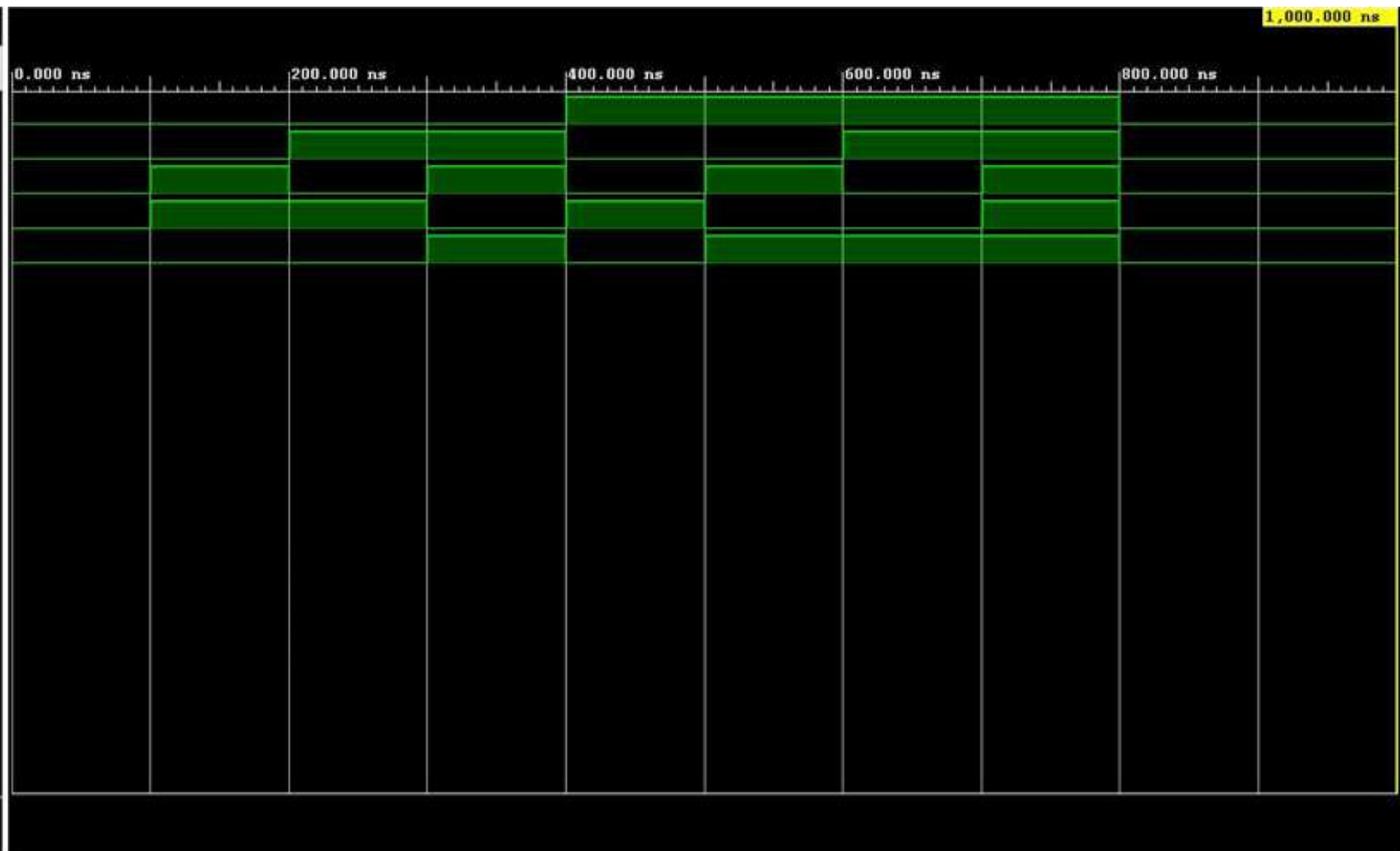

ELABORATED DESIGN - xc7a35tcpg236-1

- Project Summary x Schematic x fulladder\_2to1.v x ? [ ]

- 
 7 Cells   5 I/O Ports   12 Nets

- ist 

- |     | mux    | 2tol   |
|-----|--------|--------|
| 1   | 0.0000 | 0.0000 |
| 2   | 0.0000 | 0.0000 |
| 3   | 0.0000 | 0.0000 |
| 4   | 0.0000 | 0.0000 |
| 5   | 0.0000 | 0.0000 |
| 6   | 0.0000 | 0.0000 |
| 7   | 0.0000 | 0.0000 |
| 8   | 0.0000 | 0.0000 |
| 9   | 0.0000 | 0.0000 |
| 10  | 0.0000 | 0.0000 |
| 11  | 0.0000 | 0.0000 |
| 12  | 0.0000 | 0.0000 |
| 99  | 0.0000 | 0.0000 |
| 100 | 0.0000 | 0.0000 |

[illegible]

fulladder\_2to1 - [C:/Users/raghava guptha/fulladder\_2to1/fulladder\_2to1.xpr] - Vivado 2023.2

File Edit Flow Tools Reports Window Layout View Help Q- Quick Access Ready

Flow Navigator

- PROJECT MANAGER
  - Settings
  - Add Sources
  - Language Templates
  - IP Catalog
- IP INTEGRATOR
  - Create Block Design
  - Open Block Design
  - Generate Block Design
- SIMULATION
  - Run Simulation
- RTL ANALYSIS
  - Run Linter
  - Open Elaborated Design
    - Report Methodology
    - Report DRC
    - Report Noise
  - Schematic

ELABORATED DESIGN - xc7a35tcbg236-1

Sources

Netlist

Source File Properties

Project Summary x Schematic x fulladder\_2to1.v x

C:/Users/raghava guptha/fulladder\_2to1/fulladder\_2to1.srcs/sources\_1/new/fulladder\_2to1.v

```
1 module mux_2to1(i, s, y);
2     input [1:0] i;
3     input s;
4     output reg y;
5
6     always @(*) begin
7         if (s == 0)
8             y = i[0];
9         else
10            y = i[1];
11        end
12    endmodule
13
14 module fa(a, b, cin, s, ca);
15     input a, b, cin;
16     output s, ca;
17     wire [3:0] w;
18
19     mux_2to1 m1({~cin, cin}, b, w[0]);
20     mux_2to1 m2({cin, ~cin}, b, w[1]);
21     mux_2to1 m3({w[1], w[0]}, a, s);
22     mux_2to1 m4({cin, 1'b0}, b, w[2]);
23     mux_2to1 m5({1'b1, cin}, b, w[3]);
24     mux_2to1 m6({w[3], w[2]}, a, ca);
25 endmodule
```

Tcl Console Messages Log Reports Design Runs