

Name	Value
> i[3:0]	0
o[15:0]	0001
o[15]	0
o[14]	0
o[13]	0
o[12]	0
o[11]	0
o[10]	0
o[9]	0
o[8]	0
o[7]	0
o[6]	0
o[5]	0
o[4]	0
o[3]	0
o[2]	0
o[1]	0
o[0]	1



4to16_using3to8 - [C:/Users/raghava guptha/4to16_using3to8/4to16_using3to8.xpr] - Vivado 2023.2

File Edit Flow Tools Reports Window Layout View Help Q- Quick Access Ready

Flow Navigator

- PROJECT MANAGER
 - Settings
 - Add Sources
 - Language Templates
 - IP Catalog
- IP INTEGRATOR
 - Create Block Design
 - Open Block Design
 - Generate Block Design
- SIMULATION
 - Run Simulation
- RTL ANALYSIS
 - Run Linter
 - Open Elaborated Design
 - Report Methodology
 - Report DRC
 - Report Noise
 - Schematic

ELABORATED DESIGN - xc7a35tcpg236-1

Project Summary x Schematic x 4to16_3to8.v * x

3 Cells 20 I/O Ports 21 Nets

The schematic diagram illustrates a 4-to-16 bit decoder implemented using two 3-to-8 decoders (labeled d1 and d2). The input $i[3:0]$ is connected to a 4-bit bus. The least significant bit of this input, $i[0]$, is connected to the enable input ($en0_i$) of an inverter block labeled RTL_INV . The output of the inverter, O , is connected to the enable input (en) of both decoder blocks $d1$ and $d2$. The remaining three bits of the input, $i[2:0]$, are connected to the data input ($i[2:0]$) of both decoder blocks. The output of decoder $d1$ is $o[7:0]$, and the output of decoder $d2$ is also $o[7:0]$. These two 8-bit outputs are concatenated to form the final 16-bit output $o[15:0]$.

Tcl Console Messages Log Reports Design Runs

Hot days ahead 84°F

Search

7:58 PM 6/15/2025

4to16_using3to8 - [C:/Users/raghava guptha/4to16_using3to8/4to16_using3to8.xpr] - Vivado 2023.2

FileEditFlowToolsReportsWindowLayoutViewHelpQ- Quick Access

Ready

Default Layout

Flow Navigator

PROJECT MANAGER

Settings

Add Sources

Language Templates

IP Catalog

IP INTEGRATOR

Create Block Design

Open Block Design

Generate Block Design

SIMULATION

Run Simulation

RTL ANALYSIS

Run Linter

Open Elaborated Design

Report Methodology

Report DRC

Report Noise

Schematic

ELABORATED DESIGN - xc7a35tcbg236-1

Project SummarySchematic4to16_3to8.v*

C:/Users/raghava guptha/4to16_using3to8/4to16_using3to8.srscs/sources_1/new/4to16_3to8.v

5always @(*)

6begin

7if (en == 1'b1)

8begin

9case(i)

103'b000: o = 8'b00000001;

113'b001: o = 8'b00000010;

123'b010: o = 8'b00000100;

133'b011: o = 8'b00001000;

143'b100: o = 8'b00010000;

153'b101: o = 8'b00100000; // Fixed duplicate value

163'b110: o = 8'b01000000; // Fixed incorrect value

173'b111: o = 8'b10000000;

18endcase

19end

20else

21o = 8'b00000000;

22end

23endmodule

24module dec4to16_dec3to8(i, o);

25input [3:0] i;

26output [15:0] o;

27dec_3to8 d1(i[2:0], o[7:0], ~i[3]);

28dec_3to8 d2(i[2:0], o[15:8], i[3]);

29endmodule

Tcl ConsoleMessagesLogReportsDesign Runs

1:5

Insert

Verilog

Hot days ahead
84°F

Search

ENG
IN

7:58 PM
6/15/2025

4to16_using3to8 - [C:/Users/raghava guptha/4to16_using3to8/4to16_using3to8.xpr] - Vivado 2023.2

FileEditFlowToolsReportsWindowLayoutViewHelpQ- Quick Access

Flow Navigator

PROJECT MANAGER

Settings

Add Sources

Language Templates

IP Catalog

IP INTEGRATOR

Create Block Design

Open Block Design

Generate Block Design

SIMULATION

Run Simulation

RTL ANALYSIS

Run Linter

Open Elaborated Design

Report Methodology

Report DRC

Report Noise

Schematic

ELABORATED DESIGN - xc7a35tcbg236-1

Project Summary xSchematic x4to16_3to8.v* x

C:/Users/raghava guptha/4to16_using3to8/4to16_using3to8.srscs/sources_1/new/4to16_3to8.v

1 module dec_3to8(i, o, en);
2 input [2:0] i;
3 input en;
4 output reg [7:0] o;
5 always @(*)
6 begin
7 if (en == 1'b1)
8 begin
9 case(i)
10 3'b000: o = 8'b00000001;
11 3'b001: o = 8'b00000010;
12 3'b010: o = 8'b00000100;
13 3'b011: o = 8'b00001000;
14 3'b100: o = 8'b00010000;
15 3'b101: o = 8'b00100000; // Fixed duplicate value
16 3'b110: o = 8'b01000000; // Fixed incorrect value
17 3'b111: o = 8'b10000000;
18 endcase
19 end
20 else
21 o = 8'b00000000;
22 end
23 endmodule
24 module dec4to16_dec3to8(i, o);
25 input [3:0] i;
26 output [15:0] o;

Tcl ConsoleMessagesLogReportsDesign Runs

1:5

Insert












 





 
 
Verilog

Hot days ahead
84°F

Search

ENG IN

7:58 PM
6/15/2025

Name	Value
>  i[3:0]	0
 en	1
✓  o[15:0]	8000
 [15]	1
 [14]	0
 [13]	0
 [12]	0
 [11]	0
 [10]	0
 [9]	0
 [8]	0
 [7]	0
 [6]	0
 [5]	0
 [4]	0
 [3]	0
 [2]	0
 [1]	0
 [0]	0



4to16_using2to4 - [C:/Users/raghava guptha/4to16_using2to4/4to16_using2to4.xpr] - Vivado 2023.2

File Edit Flow Tools Reports Window Layout View Help Q- Quick Access

Ready

Default Layout

Flow Navigator

ELABORATED DESIGN - xc7a35tcbg236-1

Project Summary x Schematic x 4to16_2to4.v * x

5 Cells 21 I/O Ports 25 Nets

The schematic diagram illustrates a 4-to-16 bit decoder implemented using four 2-to-4 decoders (labeled d1, d2, d3, d4, and d5). The input is a 4-bit signal $i[3:0]$ and an enable signal en . The output is a 16-bit signal $o[15:0]$. The decoders are connected as follows: d1 takes $i[3:0]$ and en as inputs and outputs $o[3:0]$. d2, d3, d4, and d5 each take $o[3:0]$ and en as inputs and output $o[3:0]$. The outputs of d2, d3, d4, and d5 are connected to the output $o[15:0]$.

Tcl Console Messages Log Reports Design Runs

4to16_using2to4 - [C:/Users/raghava guptha/4to16_using2to4/4to16_using2to4.xpr] - Vivado 2023.2

File Edit Flow Tools Reports Window Layout View Help

Q Quick Access

Ready

Default Layout

Flow Navigator

PROJECT MANAGER

Settings

Add Sources

Language Templates

IP Catalog

IP INTEGRATOR

Create Block Design

Open Block Design

Generate Block Design

SIMULATION

Run Simulation

RTL ANALYSIS

Run Linter

Open Elaborated Design

Report Methodology

Report DRC

Report Noise

Schematic

ELABORATED DESIGN - xc7a35tcbg236-1

Project Summary x Schematic x 4to16_2to4.v* x

C:/Users/raghava guptha/4to16_using2to4/4to16_using2to4.srscs/sources_1/new/4to16_2to4.v

Q

1 module dec_2to4(a, b, en, o);

2 input a, b, en;

3 output reg [3:0] o;

4 always @(*)

5 begin

6 if (en == 1'b1)

7 begin

8 case({a, b})

9 2'b00: o = 4'b0001;

10 2'b01: o = 4'b0010;

11 2'b10: o = 4'b0100;

12 2'b11: o = 4'b1000;

13 endcase

14 end

15 else

16 o = 4'b0000;

17 end

18 endmodule

19 module dec4to16_dec2to4(i, o, en);

20 input [3:0] i;

21 input en;

22 output [15:0] o;

23 wire [3:0] w; // First stage decoder (decodes upper 2 bits)

24 dec_2to4 d1(i[3], i[2], en, w); // Second stage decoders (decode lower 2 bits)

25 dec_2to4 d2(i[1], i[0], w[0], o[3:0]);

26 dec_2to4 d3(i[3], i[2], w[1], o[7:4]);

27 dec_2to4 d4(i[1], i[0], w[1], o[11:8]);

28 dec_2to4 d5(i[3], i[2], w[1], o[15:12]);

29 endmodule

Tcl Console Messages Log Reports Design Runs

1:8

Insert

Verilog

83°F

Partly cloudy

Search

7:54 PM

6/15/2025